

**Electricity /
Electrodynamics
Survey**

Agenda: Energy Conversion and Transformation

Work and other Energy Forms

Potential and kinetic energy,
Molecular binding and rearrangement energies,
pV work, kinetic energy equilibration, heat flow,
Mechanical equivalent of heat,
Basic fluid dynamics, laminar & turbulent flow, (→later)


Basic Electricity

Static electric, electro-magnetic phenomena,
Electromagnetic induction, generators, transformers,
Electrical current laws, AC/DC transmission,
Electronic circuits, reactance,

Principles of Thermodynamic Processes

Laws of Thermodynamics, state functions, reversible processes,
Carnot and other TD cycles, steam engines, gas turbines,
Electro-chemistry, batteries, hydrolyzers & fuel cells.

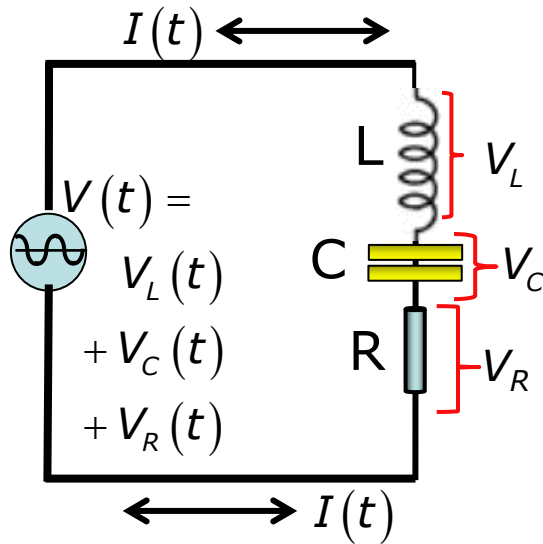Basic Electrical Network Conservation Laws



$$V(t) = V_L(t) + V_C(t) + V_R(t)$$

Kirchhoff's Loop (or mesh) Rule

The directed sum of the potential differences (voltages) over circuit elements is zero around any closed loop.

$$\text{Ohm's Law } V(t) = Z \cdot I(t + \Delta t_\phi)$$


$(\Delta t_\phi \leftarrow \Delta\phi_I = \text{phase difference } I \text{ rel } V)$

1. Ohm resistance $Z = \text{Re}(Z) = R$
2. Capacitive reactance $X_C = -1/\omega C$ ($\Delta\phi_I = +90^\circ$)
3. Inductive reactance $X_L = \omega L$ ($\Delta\phi_I = -90^\circ$)

$$I(t) = I_L(t) + I_C(t) + I_R(t)$$

Kirchhoff's Junction Rule for currents (Parallel Loops)

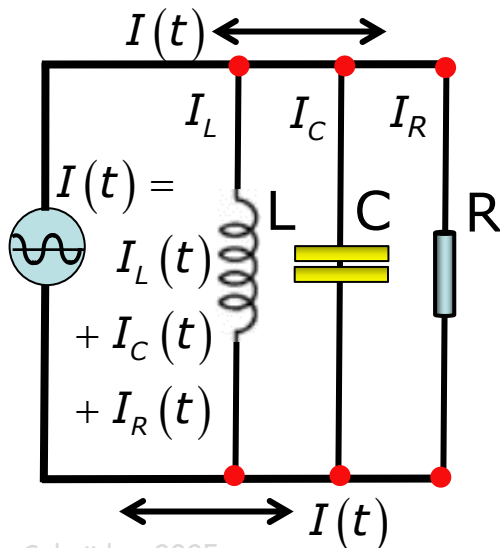The algebraic sum of currents in a network of conductors meeting at a point is zero.



Complex Notation

Phase differences are conveniently handled in complex notation $V(t)$, $I(t)$

$$V(t) = |V(t)| \cdot e^{i(\omega \cdot t + \phi_V)}; \quad I(t) = |I(t)| \cdot e^{i(\omega \cdot t + \phi_I)}$$

Amplitudes and phases are determined from initial conditions, $V(t=0)$, $I(t=0)$.

Example: $V(t=0) = V_0 \rightarrow V(t) = V_0 \cdot \cos(\omega \cdot t)$

Ohm's Law $V(t) = Z \cdot I(t + \Delta t_\phi)$ in circuits at all times

Impedance $Z(\omega) = R + i \cdot [X_C(\omega) + X_L(\omega)] \quad (i := \sqrt{-1})$


1. Ohm resistance R
2. Capacitive reactance $X_C = -1/\omega C$ ($\Delta\phi_I = +90^\circ$)
3. Inductive reactance $X_L = \omega L$ ($\Delta\phi_I = -90^\circ$)



Euler's Formula: $i = e^{i \cdot \pi/2} = \cos(\pi/2) + i \cdot \sin(\pi/2)$

Real and Reactive Power

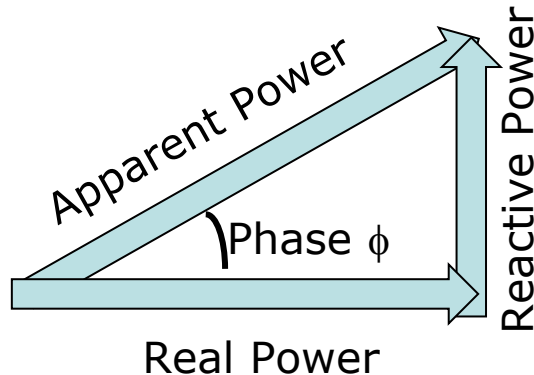Power $P(t) = V(t) \cdot I(t)$ or, in complex notation $P = V \cdot I^*$ (* = complex conjugate)



Real (Ohm) resistive loads : $P_R = V_R \cdot I = V^2/R = I^2 \cdot R$

Real = apparent power $P_R(t) = V_R(t) \cdot I(t)$ $[P_R] = W$

Oscillating reactive power $P_C(t) \Leftrightarrow P_L(t)$

Reactive power $P_{LC}(t) = |P_A(t)| \cdot \sin \phi$

"var" voltage – ampere – reactive

Complex : *Real and reactive power are "out of phase"*

Apparent power : $P_A^2(t) = P_R^2(t) + [P_C^2(t) + P_L^2(t)]$


In General : Apparent power $P_A(t) = \sqrt{P_R^2(t) + P_{LC}^2(t)}$

Useful real power $P_R(t) = |P_A(t)| \cdot \cos \phi \rightarrow$ *Power Factor* = $P_R / |P_A|$

Actual loads on the power supply (e-grid) like an e-motor are always complex (Ohm + capacitive + inductive) \rightarrow have feedback effect on supply \rightarrow Affect power factor (available power) and frequency.

\rightarrow **General effect on stability of grid.**

Effect of Reactance in AC System

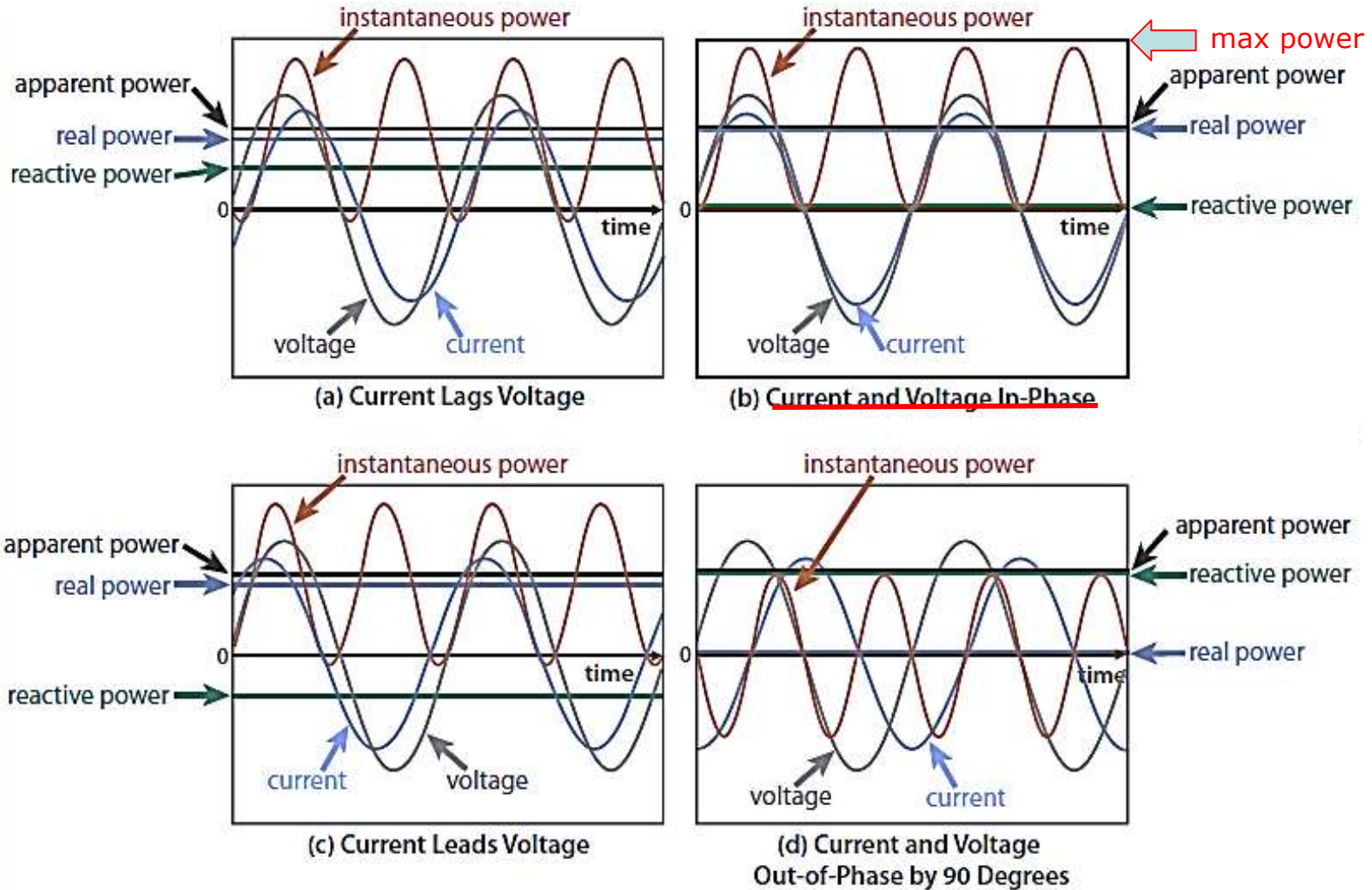

Components of Electrical DC Circuits: Resistors

Electric current I unit=[1 A(mpere)= 1C/s]:


e^- stream [$dq/dt=\#e^-/\text{sec}$] transfers power through metallic wires, dissipates e^- energy \rightarrow heat. All metallic wires have intrinsic (distributed) resistivity $\neq 0$.

Always finite electric conductivity $\sigma =$ inverse of resistivity $\rho \neq 0 !!$


$$[\sigma] = \left(\frac{A}{m^2} \right) / \left(\frac{V}{m} \right)$$

$$= (A/V)/m = 1/\Omega \cdot m$$

$$[\rho] = \Omega \cdot m$$

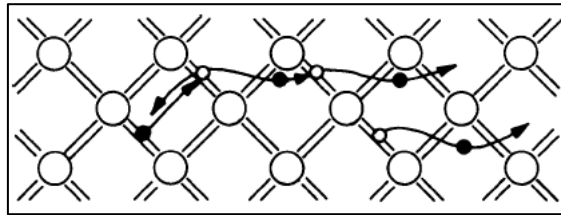

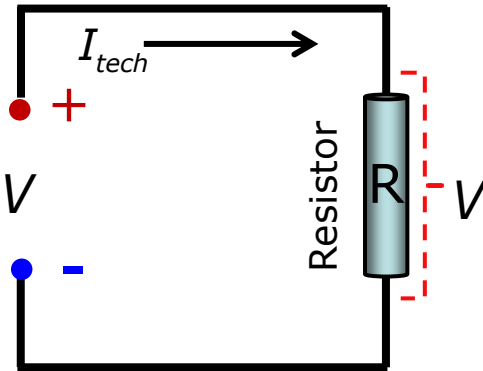Multiple scattering of e^- in lattice of R



Ohm's Law, R real (no ω dependence)

$$I = \frac{V}{R} \rightarrow V = I \cdot R$$

$$[R] = 1\Omega \text{ (Ohm)} = \frac{1V}{1A}$$

Commercial resistors are made of materials with high electric resistivity ρ .
Ref. Cu: $\rho = 1.68 \cdot 10^{-8} \Omega m$

Power dissipated in resistor (*Temp* \nearrow)

$$P = V \cdot I = I^2 \cdot R \quad [P] = W \text{ (Watt)} = J/s$$

Components of Electrical AC Networks: Resistors


Transfer of electrical power through metallic wires \rightarrow Electric conductivity $\sigma \rightarrow$ **Electrons dissipate kinetic energy** through scattering
 \rightarrow Ohm resistance $R \sim 1/\sigma$ $[R] = \Omega$ (Ohm) **Extension:** R =generic workload

Applied AC voltage $[V] = V$ (Volt)

$$V(t) = V_{\max} \cos(\omega t) \rightarrow \text{effective } V = \langle V(t) \rangle = V_{\max} / \sqrt{2}$$

$$\text{effective } I = \langle I(t) \rangle = I_{\max} / \sqrt{2}$$

Averaged
over 1 period

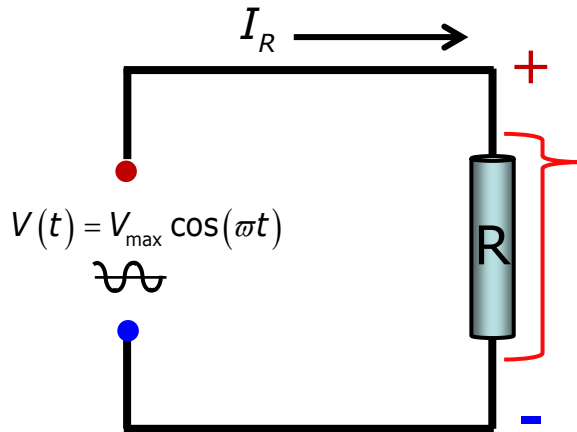

$$I_R(t) = I_{\max} \cos(\omega t); \quad I_{\max} = \frac{V_{\max}}{R} \quad \text{Ohm's Law}$$

Current $I_R(t)$ $\{[I] = A$ (Ampere) $\}$ *in phase with $V(t)$*

Power dissipated in resistor via scattering

$$P_R(t) = V(t) \cdot I_R(t) = V_{\max} I_{\max} \cos^2(\omega t)$$


$$= \frac{1}{2} V_{\max} I_{\max} \{1 + \cos(2\omega t)\} = V \cdot I_R \{1 + \cos(2\omega t)\}$$

effective

$$\text{Dissipated power } \langle P_R(t) \rangle = V \cdot I_R = \frac{V^2}{R} = I_R^2 \cdot R$$

This is real power loss, dissipated into heat (no w).

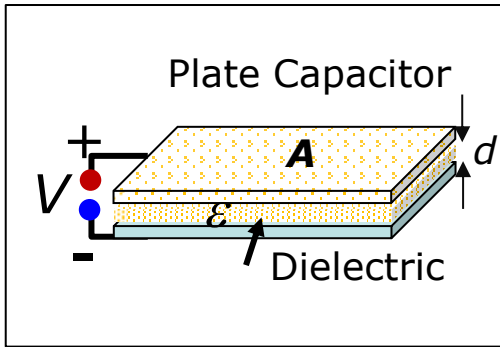Components of Electrical DC Circuits: Capacitors




Metal plates (area A) separated by dielectric medium (ϵ) of thickness d form a capacitor w. **capacitance**

$$C = \frac{\epsilon \cdot A}{d} \quad [C] = F (\text{Farad})$$

→ Carries charge

$$Q(t) = C \cdot V(t)$$

As "load" element :

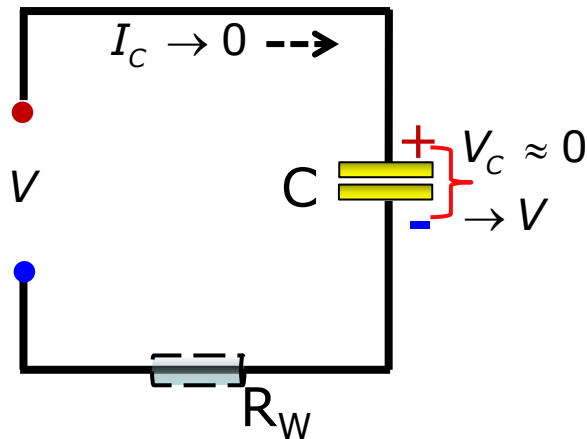

Switch – on voltage $V \rightarrow$ brief current $I_C(t)$

$$V_C(t) = \frac{1}{C} Q(t) = \frac{1}{C} \int I_C(t') dt' \rightarrow V_C(t) = V \cdot (1 - e^{-t/\tau})$$

Energy content W_C of capacitor C

$$W_C = \frac{1}{2} Q \cdot V = \frac{C}{2} V^2 = \frac{Q^2}{2C}$$


A purely capacitive load in an electrical circuit does not lose charge or energy.

But circuit wire conductors have always an additional $R_W \neq 0$.


→ Slow dissipation of energy content of source, t -const. $\tau = R_W \cdot C$

Components of Electrical AC Networks: Capacitors

Parallel Plate Capacitor

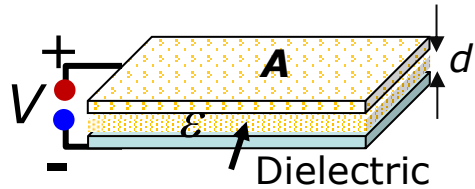
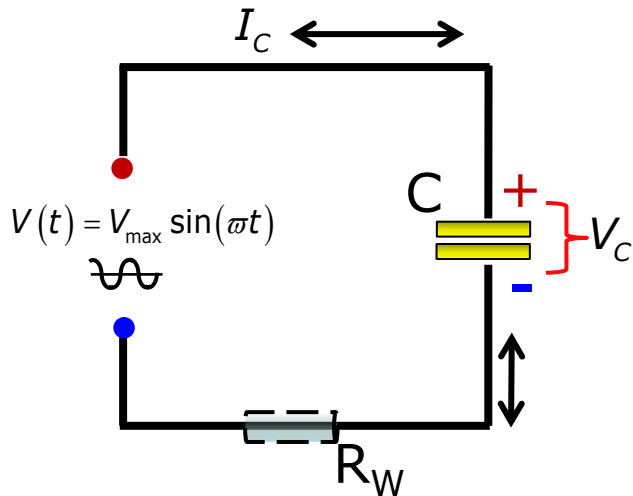
$$C = \frac{\epsilon \cdot A}{d}; [C] = F (\text{Farad})$$



Metal plates (area A) separated by dielectric medium (ϵ) of thickness d form a capacitor w. capacitance C .
As "load" element in AC (frequency ω) circuit:

→ Carries electric charge $Q(t) = C \cdot V(t)$

$$V_C(t) = \frac{1}{C} Q(t) = \frac{1}{C} \int I_C(t') dt' = \frac{I_{\max}}{\omega C} \cos(\omega t)$$

$$= V_{\max} \cos(\omega t) \rightarrow V_{\max} = I_{\max} \cdot X_C \quad \text{Ohm's Law}$$

$$\text{Reactance } |X_C| = \frac{1}{\omega C}$$

Current leads voltage : phase difference $\Delta\phi = +\frac{\pi}{2}$

Power in capacitor

$$P_C(t) = V(t) \cdot I_C(t) = V_{\max} I_{\max} \sin(\omega t) \cdot \cos(\omega t)$$

$$= \frac{1}{2} V_{\max} I_{\max} \{ \sin(2\omega t) \} \rightarrow \langle P_C(t) \rangle = 0$$

A pure capacitive load in an AC circuit does not dissipate (lose) power.

But circuit wire conductors have always an additional $R_W \neq 0$.

→ Slow dissipation of energy content of source, time-const. $\tau = R_W \cdot C$


Components of Electrical DC/AC Circuits: Inductors



Helical coil area A : N windings insulated Cu wire around core \rightarrow plastic ("solenoid") or ferrite/carbon-iron.
 Applied electric $V \rightarrow$ current I , \rightarrow static axial B field ("electro-magnet").

Inductance $L = \mu_0 K (N^2 A / \ell)_{coil}$ $[L] = H = \frac{V \cdot s}{A}$ (Henry)

As "load" element in circuit:

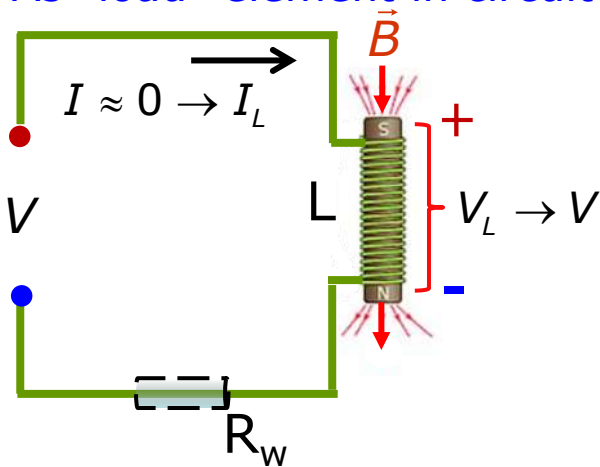

$$V_L(t) = -L \frac{dI}{dt} \rightarrow \text{Work } \frac{dW_L}{dt} = -L \cdot I \cdot \frac{dI}{dt}$$

Energy content W_L stored in inductor L

$$W_L = \frac{1}{2} L \cdot I_L^2$$

A purely inductive load in an electric circuit does not dissipate electric energy.

But circuit wire conductors have always an additional $R_w \neq 0$.

\rightarrow Slow dissipation of energy content of source, *time-const.* $\tau = L/R_w$


Components of Electrical AC Networks: Inductors



Helical coil insulated Cu wire wound around plastic ("solenoid") or ferrite/carbon-iron core. → Large resistance ($|\omega \cdot L|$) to high-frequency AC spikes.

Inductance L , $L_{solenoid} = \mu_0 K (N^2 A / \ell)_{coil}$ $[L] = H = Vs/A$ (Henry)

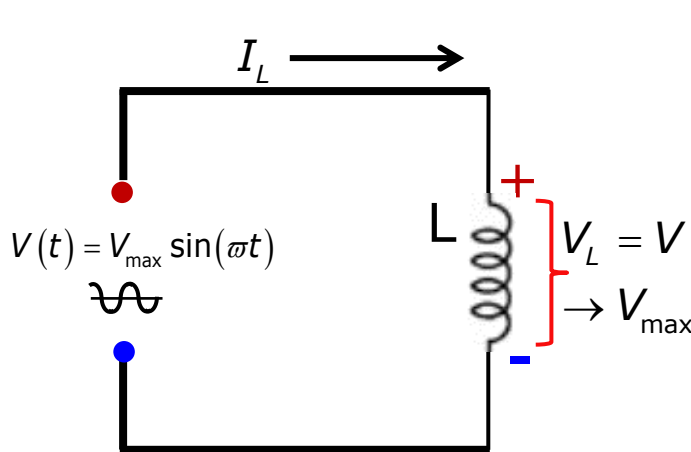As "load" element in AC (frequency ω) circuit:



$$V_L(t) = -L \frac{dI}{dt} = -\omega L \cdot I_{max} \cos(\omega t)$$

$$= V_{max} \cos(\omega t) \rightarrow V_{max} = I_{max} \cdot X_L \quad \text{Ohm's Law}$$

$$\text{Reactance } |X_L| = \omega L$$

Current lags voltage : phase difference $\Delta\phi = -\frac{\pi}{2}$


Power in inductor

$$P_L(t) = V_L(t) \cdot I(t) = -V_{max} I_{max} \sin(\omega t) \cdot \cos(\omega t)$$

$$= -\frac{1}{2} V_{max} I_{max} \{ \sin(2\omega t) \} \rightarrow \langle P_L(t) \rangle = 0$$

A pure inductive load in an AC circuit does not dissipate (lose) electric power, it moves energy between electron currents and magnetic field and changes relative phase of current vs. voltage → reactive power

Electronic LC Oscillator (E-Store)

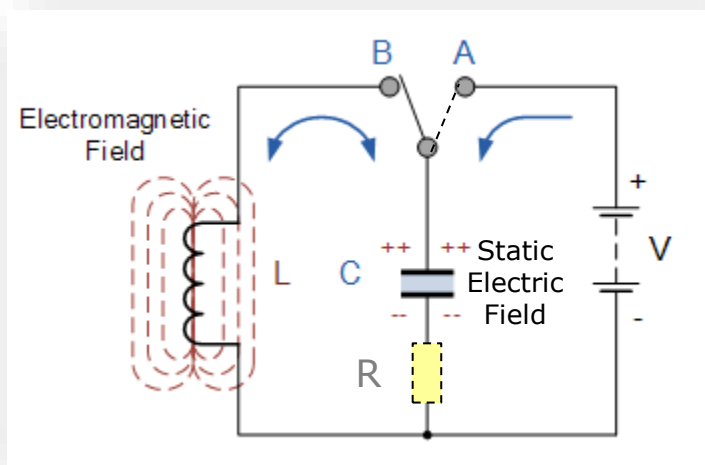

Kirchoff's Laws : Closed circuit :

$$I_C = I_L = I$$

$$V_C + V_L = 0, \quad V_C = C \cdot \frac{dI_C}{dt}, \quad V_L = L \cdot \frac{dI_L}{dt}$$

$$\text{Charge } Q(t), \quad I(t) = dQ/dt$$

$$I_C = \frac{dQ_C}{dt} = C \cdot \frac{dV_C}{dt} = I \quad (\text{Neglect } R \text{ at first})$$

$$\rightarrow I(t) = C \cdot \frac{dV_C}{dt} = -C \cdot \frac{dV_L}{dt} = -L \cdot C \cdot \frac{d^2 I}{dt^2}$$

$$\text{Define } \omega_0 := \frac{1}{\sqrt{L \cdot C}}$$

Differential Equation for **Oscillator**


$$\rightarrow \boxed{\frac{d^2 I(t)}{dt^2} + \omega_0^2 I(t) = 0} \quad \rightarrow I(t) = a \cdot e^{i(\omega_0 t + \varphi)} + b \cdot e^{-i(\omega_0 t + \varphi)}$$

Constants a, b defined by initial conditions ($t = 0$)

$$a e^{i\varphi} := \frac{I_0}{2}, \quad b e^{-i\varphi} = a^* = \frac{I_0}{2} \rightarrow I(t) = I_0 \cdot \cos(\omega_0 \cdot t)$$

Including Ohm resistance \rightarrow damped oscillations

Including Ohm Resistance R

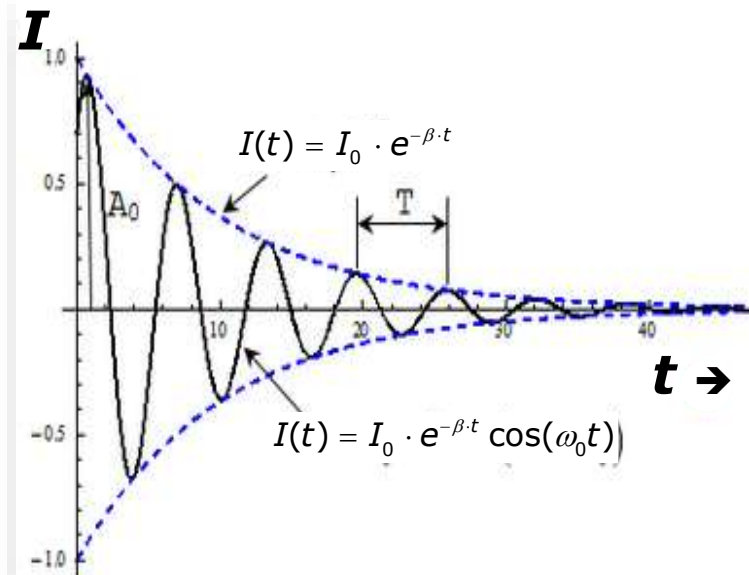

Fin Electricity

